

# Algorithm Implementation

- GPPs (Pentium) - not in this course
- VLSI
  - ASICs - not in this course
  - PLDs
    - PALs/PLAs
      - AND/OR planes
    - Gate Arrays
      - MPGAs
      - FPGAs - focus of this course

# PLDs – Programmable Logic Devices

## 1. AND/OR Arrays (PAL/PLA)

- An array of AND gates connected to an array of OR gates
- SOP form of equations
- PAL
  - AND-plane    programmable
  - OR-plane    not programmable
- PLA©
  - AND-plane    programmable
  - OR-plane    programmable

# See PLA Example

# PLDs cont

## 2. Gate Arrays

### 2.A. Mask Programmable Gate Array (MPGA)

- Arrays or rows of uncommitted, prefabricated transistors
  - Wafer is fabbed all the way except for the last metal layers
  - User submits “wire masks” to connect transistors in order to form larger circuits
  - Wafer fab is completed
  - ~ 1-2 months



### 2.B. Field Programmable Gate Arrays (FPGAs)

- Pre-fabbed programmable integrated circuit
- Completely user programmed

	FPGA	MPGA
Cost	\$	\$\$
Speed (operation)	Slower	Faster
Implementation	Immediate	Several weeks
Reprogrammability	Yes	No
  
# FPGAs - Definition

- Definition: programmable integrated circuit
- Trade-off between ASICs and general purpose processors (GPP)



# FPGAs - Advantages


- Reusable
  - ASIC => Fixed design
  - FPGA => Flexible design
- Quick circuit implementation
  - ASIC => ~ 2 months
  - FPGA => ~ 1 day
- Cheap
  - ASIC => More expensive design cycle
    - Verification
  - FPGA => Hardware verification
- Fast execution
  - GPP vs. FPGA

# FPGAs - Disadvantages

- Slow application implementation
  - FPGA vs. GPP
- Expensive
  - FPGA vs. GPP
- Slow execution
  - FPGA vs. ASIC
- Area constrained
  - Application size limited
  - Reduce size
  - Split temporally or spatially
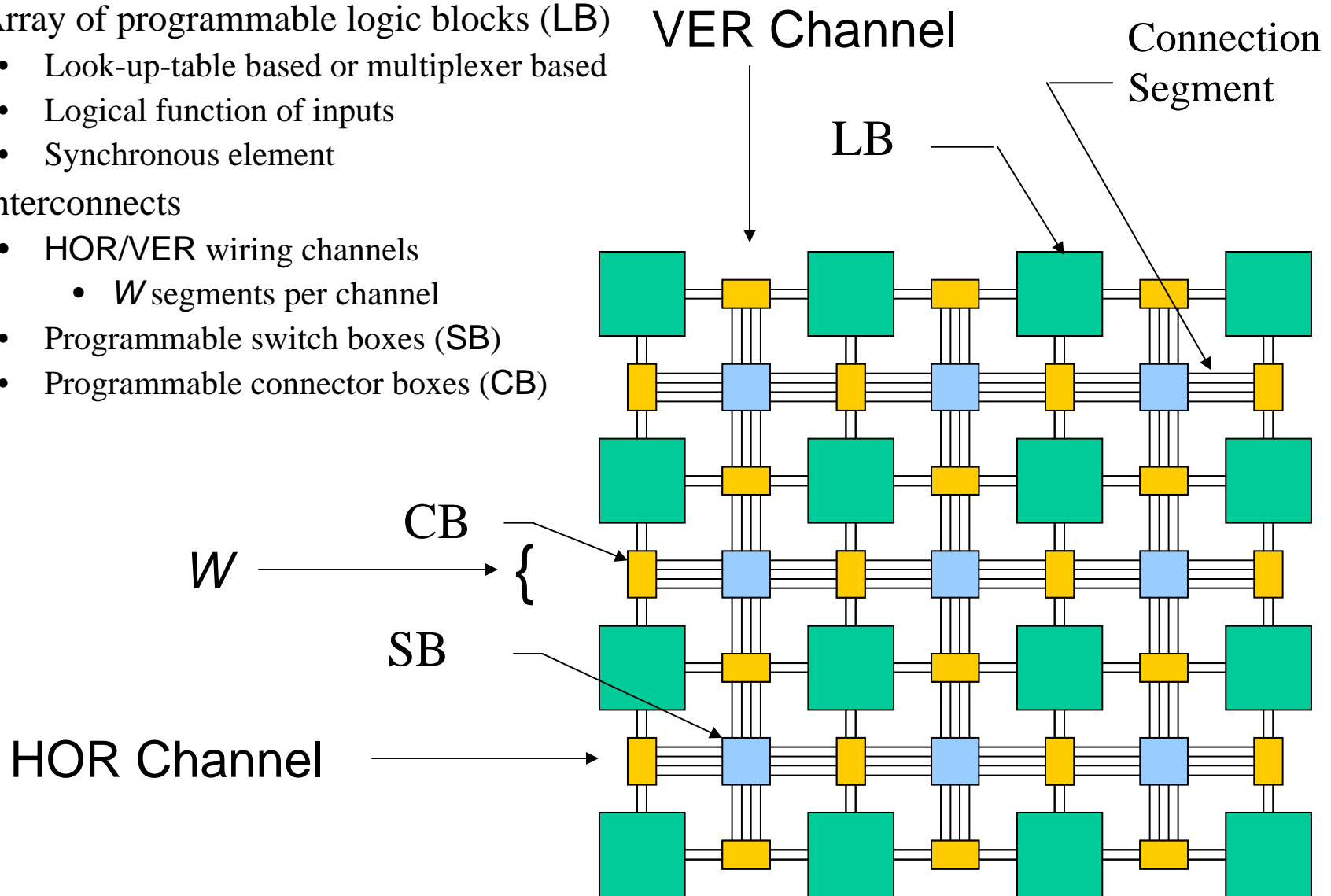
# Generic FPGA - Architecture


- Programmable IO (not shown)
- Array of programmable logic blocks (LB)
  - Look-up-table based or multiplexer based
  - Logical function of inputs
  - Synchronous element
- Interconnects
  - HOR/VER wiring channels
    - $W$  segments per channel
  - Programmable switch boxes (SB)
  - Programmable connector boxes (CB)




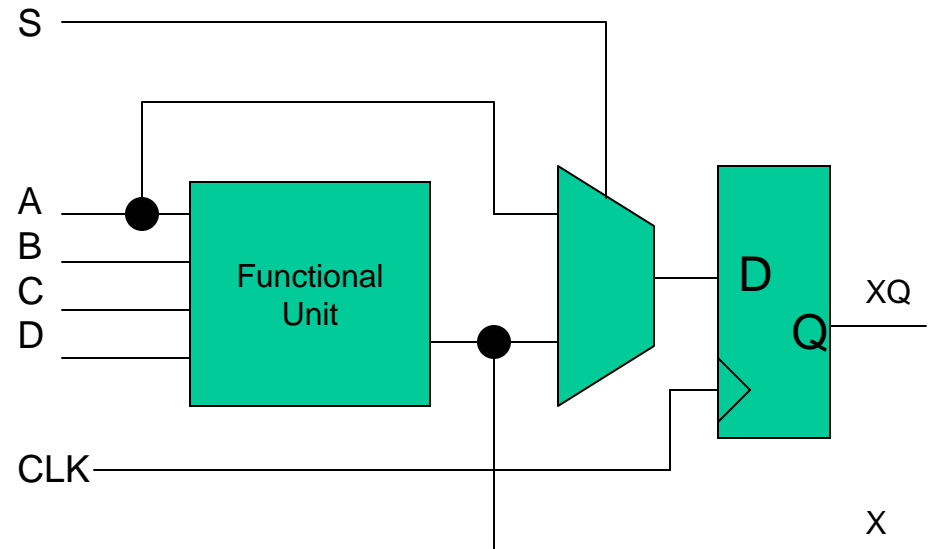
# Generic FPGA - Architecture


- PLBs or CLBs
  - Functional Unit
    - Nand Gates (PAL like)
    - Multiplexer based
    - LUT based
  - Flip-Flop
  - Usually Multiple Functional/FF units/PLB



# Generic FPGA - Architecture

- Logic blocks (LBs) Functional Unit
  - Multiplexer based
  - Look-up-table based (LUT)

$$Z = A \bullet (B + C)$$

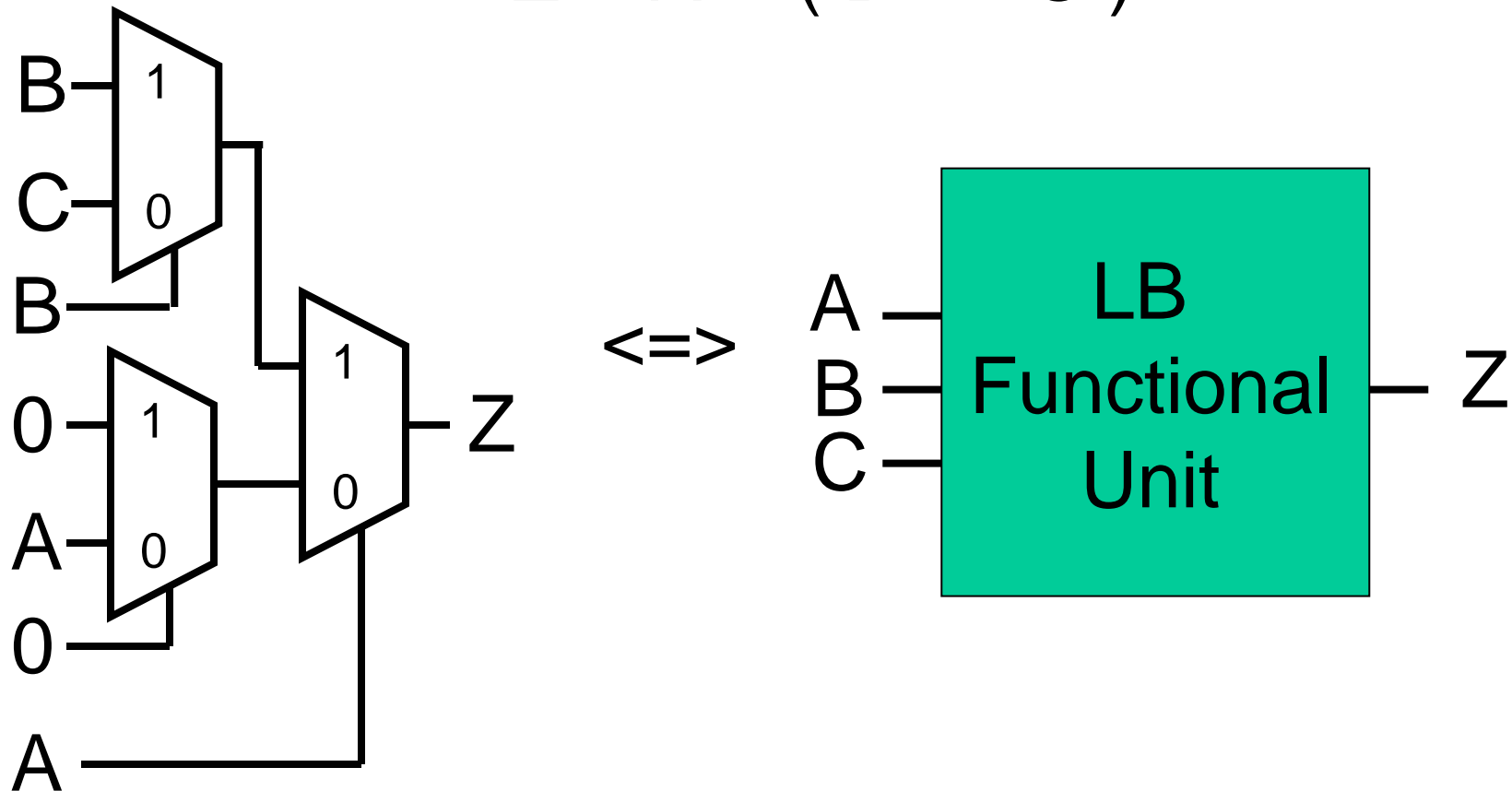


# Generic FPGA - Architecture

- Logic blocks (LBs) Functional Unit
  - Multiplexer based
  - Look-up-table based (LUT)



$$Z = A \bullet ( B + C )$$

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 
  
# Generic FPGA - Architecture

- Connector Boxes (CB)
  - Connects LB pins to connection segments
  - Flexibility  $F_C = \# \text{ possible connections} / \text{LB pin}$
- Switch Boxes (SB)
  - Connects vertical and horizontal wiring channels
  - Flexibility  $F_S = \# \text{ possible connections} / \text{incoming segment}$




# Implementation of FPGA Application

1. Initial Design Entry
2. Translation
3. Logic Optimization and Technology Mapping
4. Placement
5. Routing
6. Configuration File Generation

 
# Generic FPGA - Circuit Mapping

- 1 Design entry (synthesis,schematic capture ...)
- 2 Technology mapping
- 3 Placement
- 4 Routing
- 5 Bitmap



# Generic FPGA - Circuit Mapping

- Design entry
  - Schematic capture

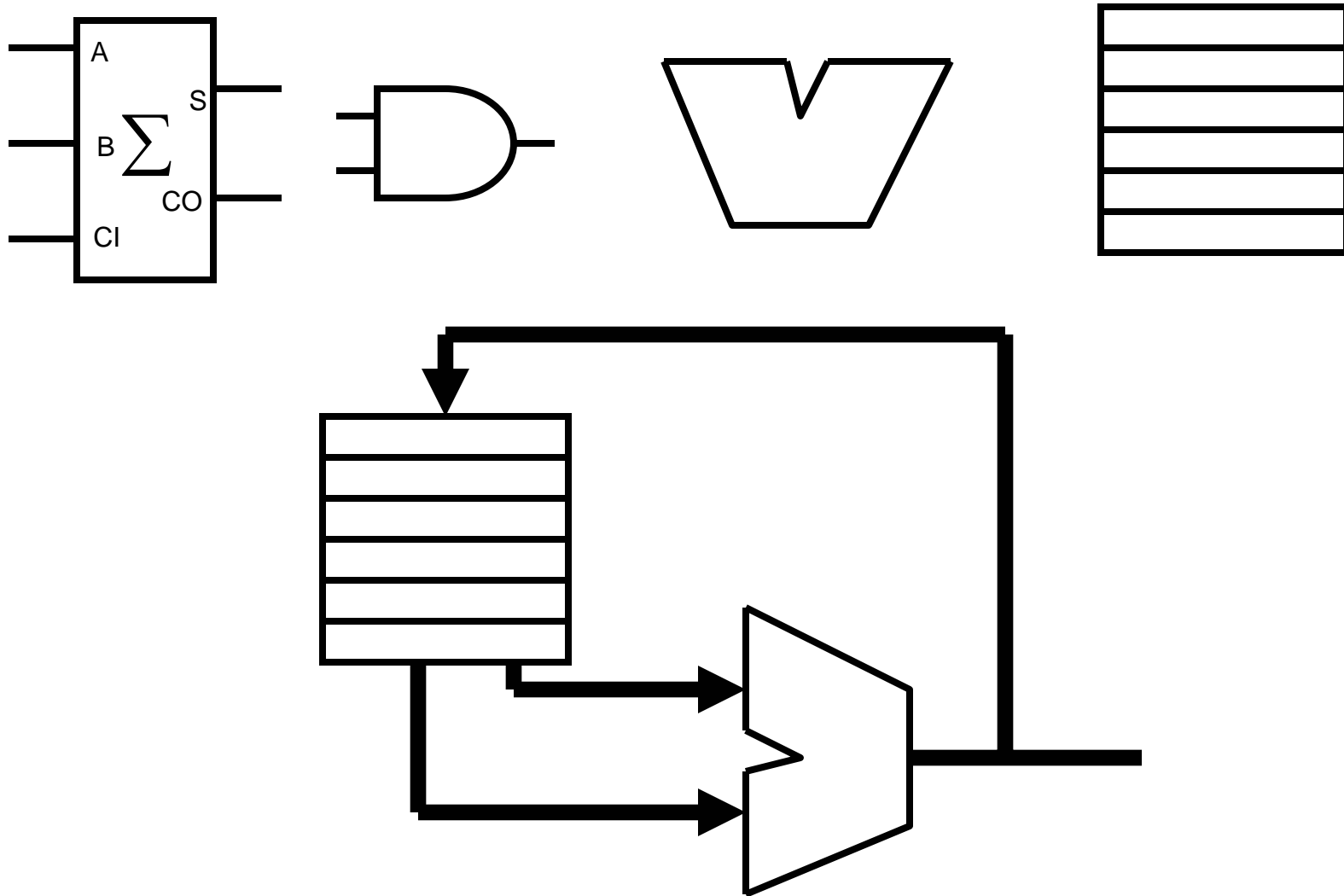

# Generic FPGA - Circuit Mapping

- Design entry
  - Synthesis VHDL or Verilog

```
entity ADDER8 is
    port(
        A : in BIT_VECTOR(7 downto 0);
        B : in BIT_VECTOR(7 downto 0);
        S : out BIT_VECTOR(8 downto 0)
    );
end;
architecture BEHAVIORAL of ADDER8 is
begin
    S <= A + B;
end;
```

•  
•  
•

$S(4) =$

$S(5) = A(5) \text{ xor } B(5) \text{ xor } C_i(5)$

$S(6) = A(6) \text{ xor } B(6) \text{ xor } C_i(6)$



# Generic FPGA - Circuit Mapping

- Technology mapping
  - Design equations  $\Rightarrow$  logic cell functions and connecting signals

$$S(4) =$$


$$S(5) = A(5) \text{ xor } B(5) \text{ xor } Ci(5)$$

$$S(6) = A(6) \text{ xor } B(6) \text{ xor } Ci(6)$$

•


•

A(6)	B(6)	Co(6)	S(6)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

 
# Generic FPGA - Circuit Mapping

- Placement
  - Physical location of logic cell functions on FPGA




# Generic FPGA - Circuit Mapping

- Routing
  - Route connecting signals

 


 
# Generic FPGA - Circuit Mapping

- Bitmap
  - Downloadable configuration file
  - Program the FPGA
  - Serial
    - 0010011101001011001010011111011101011.....
  - Parallel
    - 00100100
    - 00101101
    - ....




# Generic FPGA - Circuit Mapping

- Bitmap
  - Partial
  - Dynamic

  
 
# Generic FPGA - Circuit Mapping

- GPP with dynamically reconfigurable hardware



# Summary

- Introduction
  - Definition
  - Advantages
  - Disadvantages
- Generic architecture
  - Programmable logic blocks
  - Programmable interconnection network
    - Wiring segments
    - Switch boxes
    - Connector boxes
- Circuit mapping process
  - Design entry
  - Technology mapping
  - Placement
  - Routing
  - Configuration
- Summary